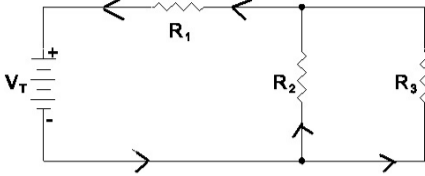
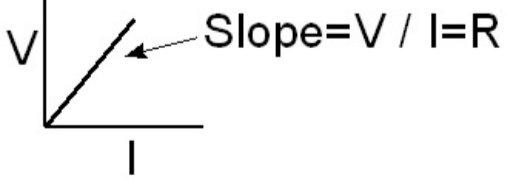
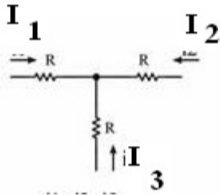
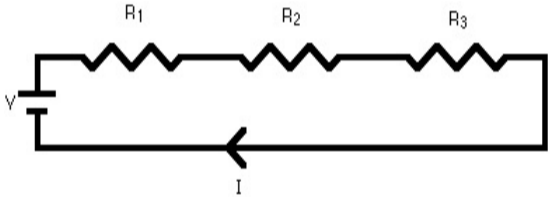
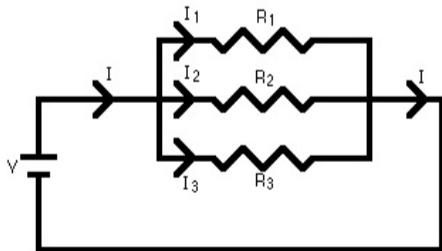


**PHYSICS 3204**  
**CURRENT ELECTRICITY**

Electron Flow	<p>Electrons flow out of the (-) terminal into the (+)</p> 
<b>CURRENT</b>	$I = \frac{Q}{t}$ <p>I = current ( ampere, A) Q = charge ( coulombs, C) λ = time (s)</p>
<b>AMMETER</b>	Instrument used to measure current. Ammeter is connected in series with the other elements of the circuit.
<b>ELECTRIC POTENTIAL ENERGY OR VOLTAGE</b>	$V = \frac{E_e}{q}$ <p>V= voltage (Volts, V) E<sub>e</sub> = Electric Potential Energy ( J) q = charge (Coulombs, C)</p>
<b>VOLTMETER</b>	The instrument used to measure voltage.
<b>ELECTRIC ENERGY</b>	$E_e = VIt$ <p>E<sub>e</sub> = Electric Potential Energy ( J) V= voltage or potential difference across the circuit ( Volts, V) I= current flowing through the circuit (Amperes, A) t = time that the circuit is being used ( seconds)</p>
<b>OHM'S LAW:</b> measures “resistance” to electron flow.	$R = \frac{V}{I}$ <p>R = resistance (Ohms, Ω) V = Voltage ( Volts, V) I = current ( ampere, A)</p>
<b>OHMIC CIRCUIT</b>	<p>when V versus I results in a straight line, the resistor has a constant resistance. Such resistors are said to be ohmic because they obey Ohm's law.</p> 

<b>FOUR FACTORS THAT AFFECT RESISTANCE:</b>	<p>1) increases in resistance as its temperature rises</p> <p>2) longer the wire, larger the resistance</p> $\frac{R_1}{R_2} = \frac{L_1}{L_2}$ <p>3) Resistance is inversely proportional to the cross-sectional area of the resistor</p> $\frac{R_1}{R_2} = \frac{L_2}{L_1}$ <p>4) Resistance is affected by the substance that makes up the resistor. ( See Resistance of Conductor below)</p>
<b>RESISTANCE OF A CONDUCTOR</b>	$R = \rho \frac{L}{A} \text{ or } R = \rho \frac{L}{\pi r^2}$ <p>R = resistance (Ohms, <math>\Omega</math>)  <math>\rho</math> = resistivity (<math>\Omega\text{m}</math>)  L = length (m)  A = Area (<math>\text{m}^2</math>)</p>
<b>KIRCHOFF'S CURRENT RULE:</b>	<p>current going into a junction point equals the current leaving the junction point.</p> $I_3 = I_1 + I_2$ 
<b>KIRCHOFF'S VOLTAGE RULE:</b>	<p>- Series (single loop) <math>V_T = V_1 + V_2</math></p> <p>- Parallel ( in every loop) <math>\Sigma V_{\text{rise}} = \Sigma V_{\text{rdrop}}</math></p>
<b>TOTAL RESISTANCE IN SERIES</b>	$R_{\text{TOTAL}} = R_1 + R_2 + R_3 + \dots$ 
<b>TOTAL RESISTANCE IN PARALLEL</b>	$\frac{1}{R_{\text{TOTAL}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$ 
<b>POWER</b>	$P = \frac{W}{t} \text{ or } P = IV$ <p>P = power ( W, watts)  W= work (J, Joules)  t = time (sec)  I= current ( amperes, A)  V = Voltage (V)</p>
<b>ENERGY</b>	$E = P/t$ <p>To find the cost of your light bill be sure to leave units as kW<math>\cdot</math>hr</p>