

Physics 3204

Core Lab -Current Electricity



Student Name: _____

Date: : _____


Purpose: For this lab activity you will use an online circuit simulator to practice building series and parallel circuits and investigate the similarities and differences between them.

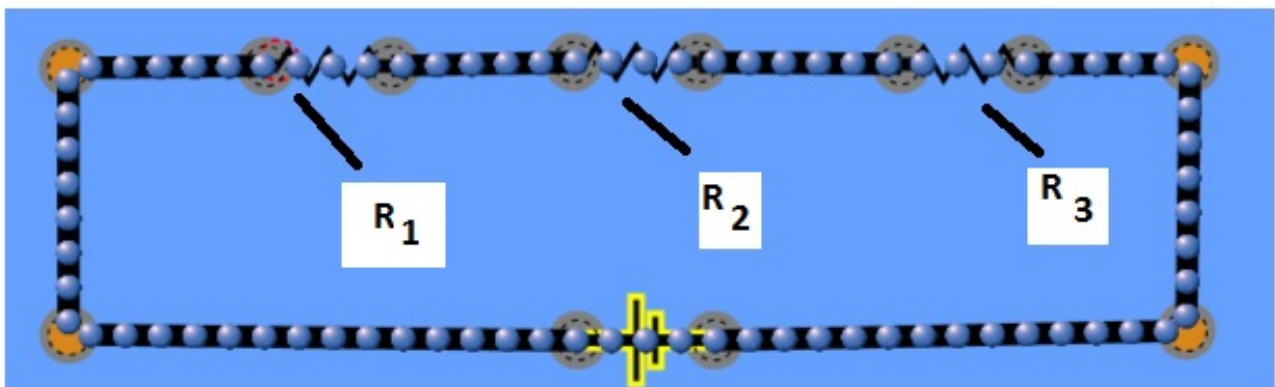PART 1: STUDY OSERIES CIRCUIT


Step #1 : Change the display to schematic by clicking it the “Visual Tab”




Step #2: Build the following series circuit



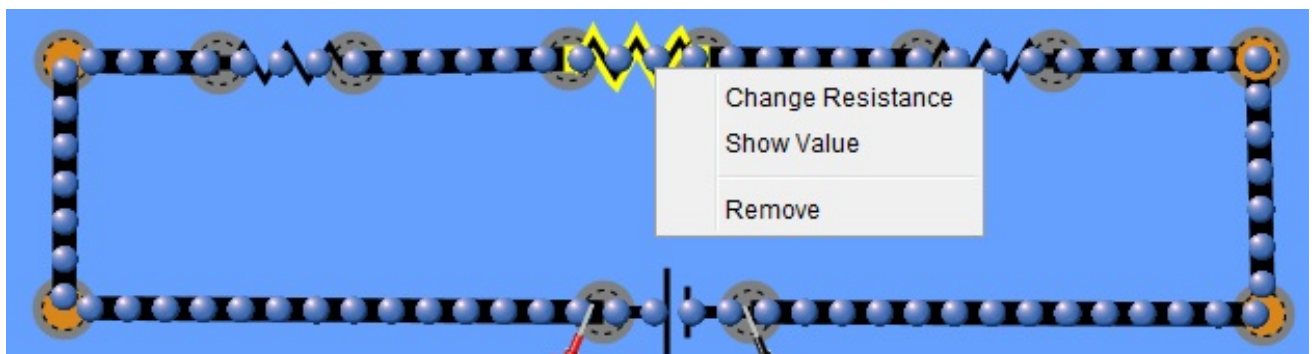
Step #3: Right click each resistor and “change resistance” to 100 Ω



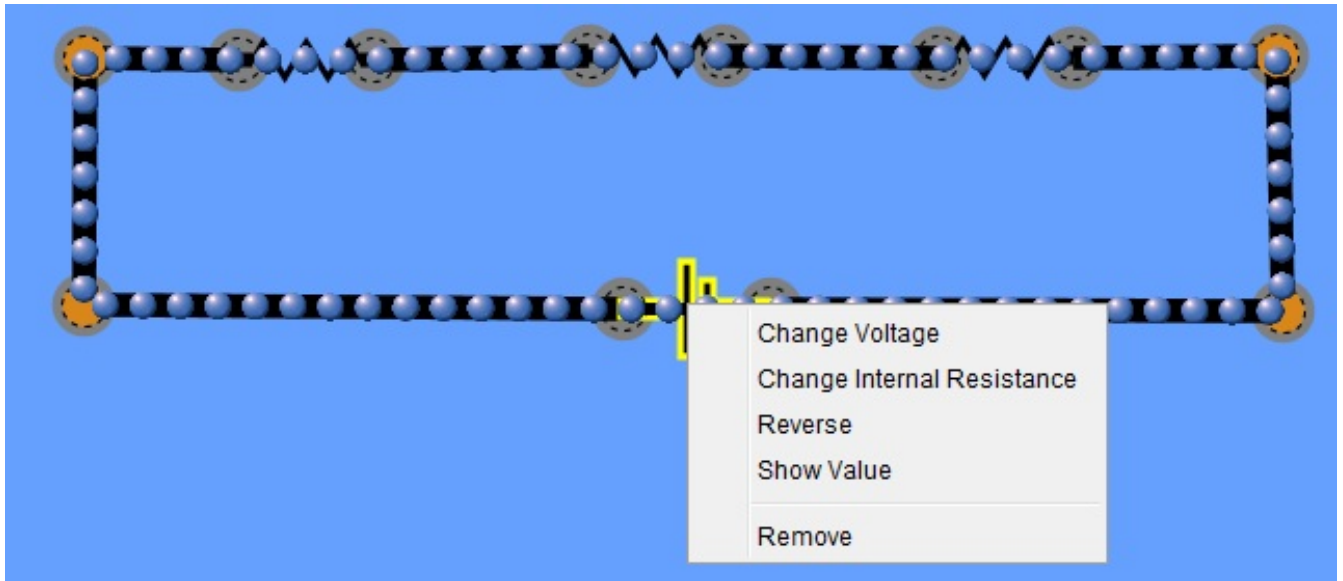Step #4: Right click the battery and “Change Voltage ” to 90 V




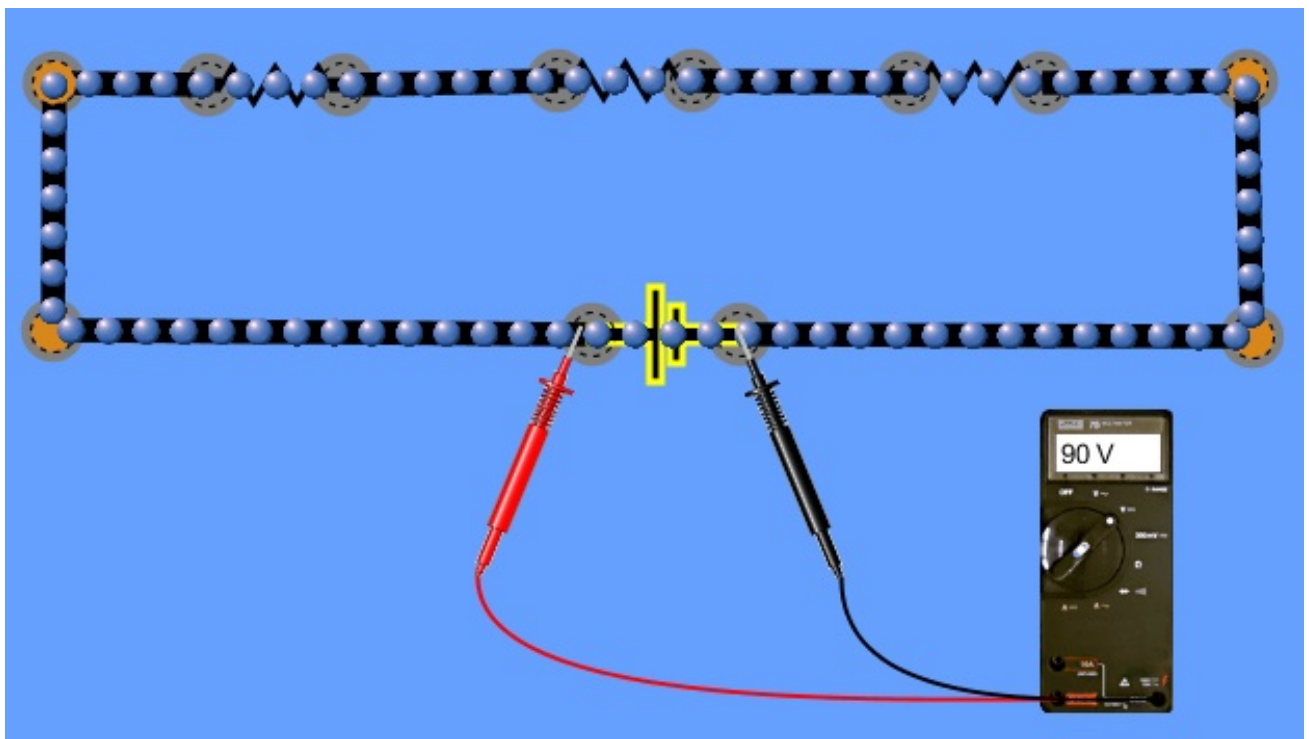Step # 5: Under tools click “Voltmeter”. Use the voltmeter as shown below to find the voltage of the battery, R_1 , R_2 and R_3 . Record your information in the table below




V_T	V_1	V_2	V_3

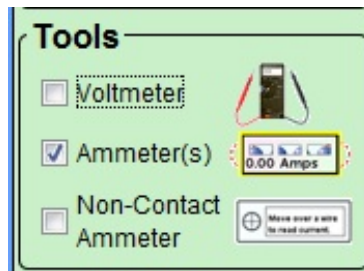
Step #6 Click the ammeter to measure the current.



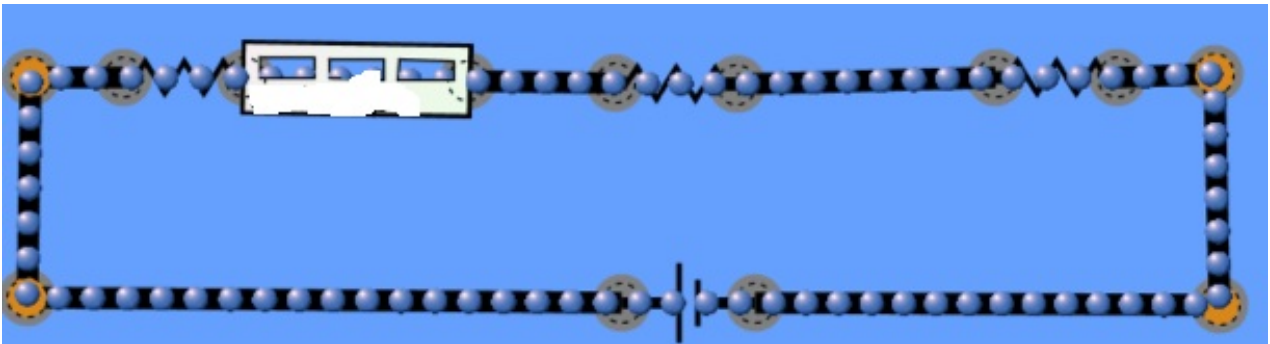Step #7: The ammeter must be put in series to measure current as shown below



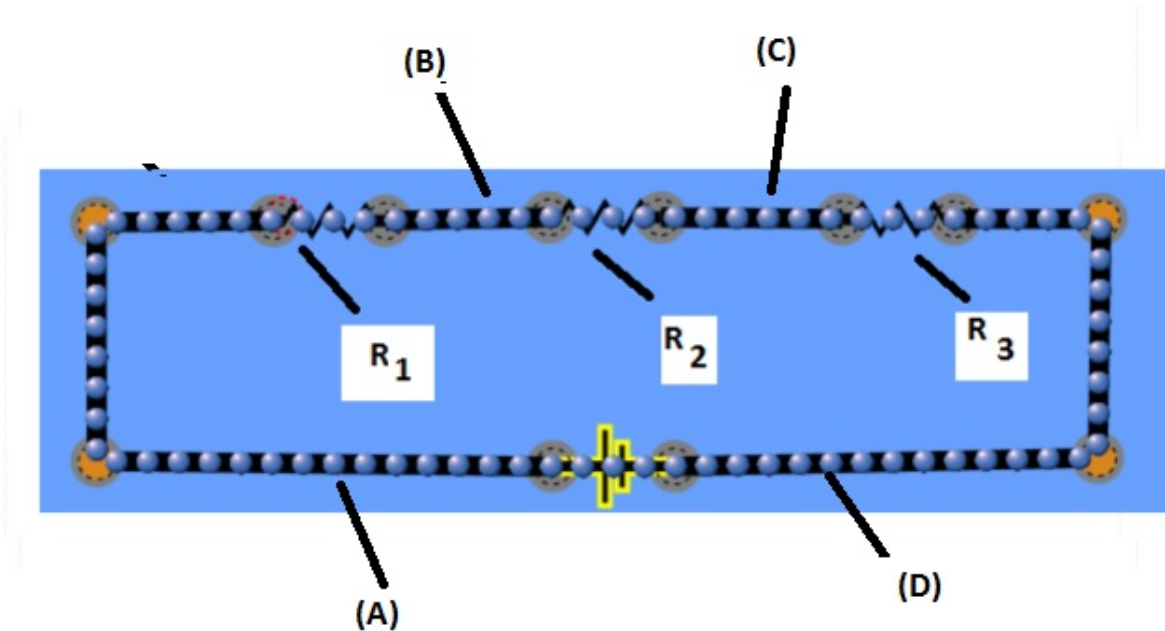Step #8: Use the ammeter to measure the current in 4 different places around the circuit as show in the picture below.



- (A) After the battery
- (B) Between R_1 and R_2
- (C) Between R_2 and R_3
- (D) Between R_3 and battery

Record your data in the table below:

Location of Measurement	Current (A)
After the battery	
Between R_1 and R_2	
Between R_2 and R_3	
Between R_3 and battery	

Question on series circuit:


1. What is the total resistance in the circuit?
2. How would you describe voltage in the series?
3. How would you describe the current in a series circuit?
4. How much power is used in this circuit.
5. This circuit is used for 3 hour daily. How much would it cost to run this circuit for a year if the rate is $\$0.12/\text{kW} \cdot \text{hr}$
6. What is one advantage of a series circuit
7. What is one disadvantage of a series circuit?

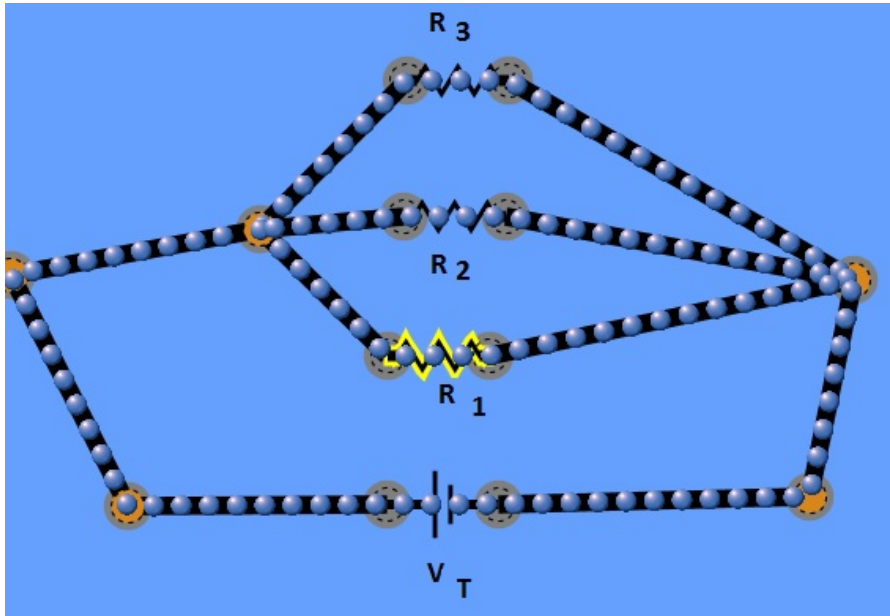PART 1: STUDY OF A PARALLEL CIRCUIT

Step #1 : Change the display to schematic by clicking it the “Visual Tab”




Step #2: Build the following parallel circuit



Step #3: Right click each resistor and “change resistance” to $100\ \Omega$


Step #4: Right click the battery and “Change Voltage ” to $90\ V$

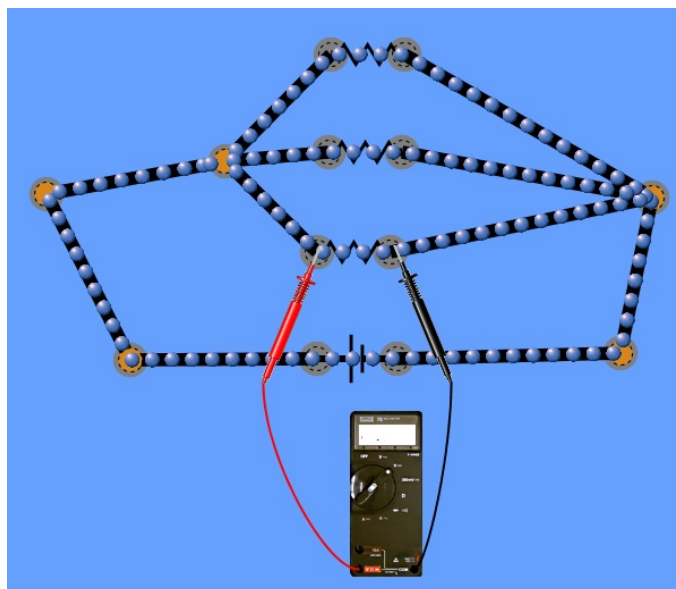Step # 5: Under tools click “Voltmeter”. Use the voltmeter as shown below to find the voltage of the battery, R_1 , R_2 and R_3 . Record your information in the table below




V_T	V_1	V_2	V_3

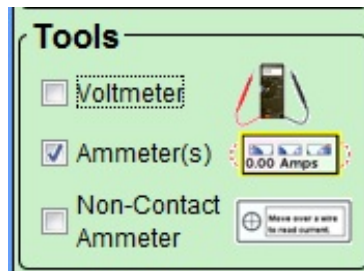
Step #6 Click the ammeter to measure the current.



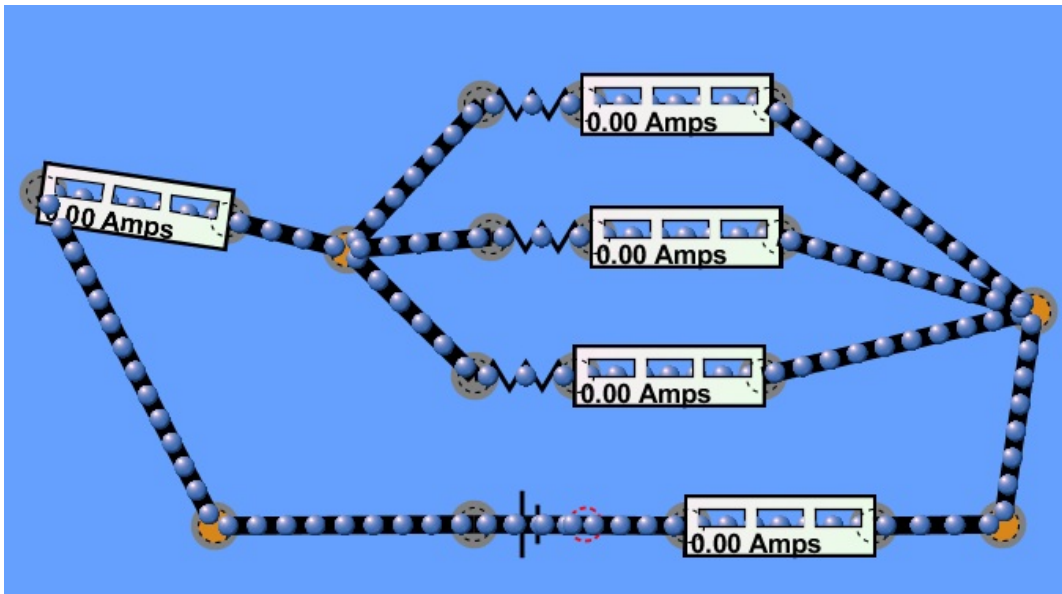Step #7: The ammeter must be put in series to measure current as shown below



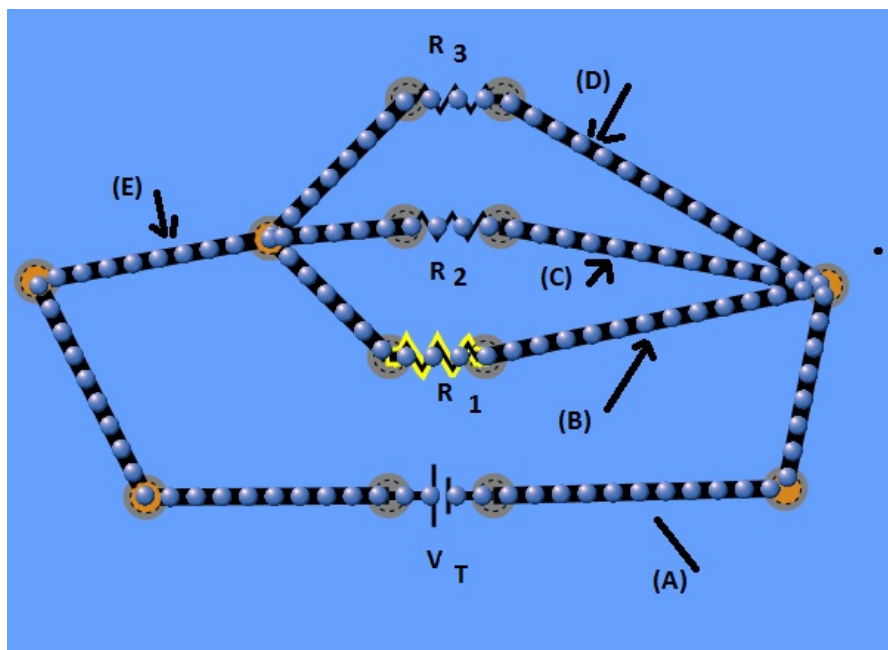Step #8: Use the ammeter to measure the current in 5 different places around the circuit as show in the picture below.



Use the ammeter to measure the following:

- (A) After the battery
- (B) Branch with R_1
- (C) Branch with R_2
- (D) Branch with R_3
- (E) After the junction point left of the resistors in parallel

Record your data in the table below:

Location of Measurement	Current (A)
After the battery	
Branch with R_1	
Branch with R_2	
Branch with R_3	
After the junction point left of the resistors in parallel	

Questions on parallel circuit:

1. What is the total resistance in the circuit?
2. How would you describe voltage in the parallel circuit ?
3. How would you describe the current in a parallel circuit?
4. How much power is used in this circuit.
5. This circuit is used for 3 hour daily. How much would it cost to run this circuit for a year if the rate is $\$0.12/\text{kW} \cdot \text{hr}$
6. What is one advantage of a parallel circuit
7. What is one disadvantage of a parallel circuit?