




Physics 3204

Unit 2: Section 2 -Current Electricity

Worksheet 6: SERIES CIRCUIT


1. For the circuit portion shown below the current through the 40Ω resistor is 0.4A . What is the current through the 10Ω resistor?

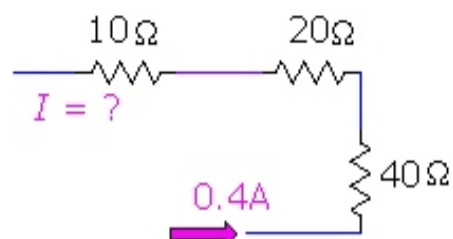- (A) 0.1 A
- (B) 0.2 A
- (C) 0.3 A
- (D) 0.4 A




2. For the circuit portion shown below the current through the 60Ω resistor is 0.6A ; the current through the 80Ω is 0.8A . What is the current through the 30Ω resistor?

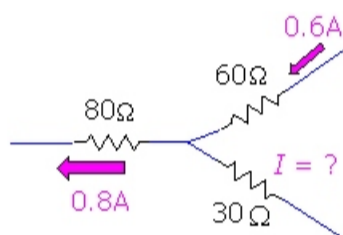- (A) 0.3 A
- (B) 0.2 A
- (C) 1.4 A
- (D) 0.6 A



3. The circuit diagram shows 3 resistors connected in series with a battery. The ammeter reads 1.5 A . What is the voltage of the battery?

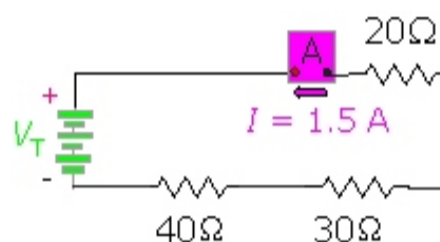- (A) 135 V
- (B) 45 V
- (C) 60 V
- (D) 14 V




4. In the diagram below an unknown resistor is connected in series with 2 known resistors. The voltage across the unknown resistor is 4V and the current through the unknown resistor is 0.2A . What is the voltage of the battery?

- (A) 34 V
- (B) 44 V
- (C) 12 V
- (D) 24 V




5. Use the information in the schematic to determine the value of R_2 .

- (A) 4Ω
- (B) 2.0Ω
- (C) 6.0Ω
- (D) 8Ω

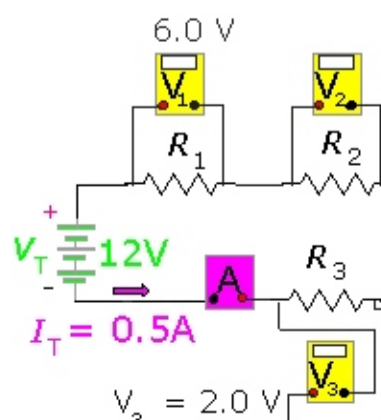

6. In the branch to the right the total resistance is T ohms. What is value of R_2 ?

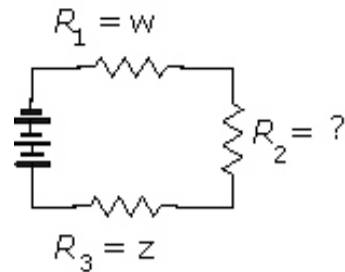- (A) $T + w + z$
- (B) $T - w - z$
- (C) $T - w + z$
- (D) $(w + z) - T$



7. If four $20\ \Omega$ resistors are connected in series, what is the equivalent resistance?


- (A) $5\ \Omega$
- (B) $10\ \Omega$
- (C) $20\ \Omega$
- (D) $80\ \Omega$

8. What is the total resistance when a $12\ \Omega$ and $15\ \Omega$ resistor are connected in parallel?

- (A) $0.037\ \Omega$
- (B) $0.15\ \Omega$
- (C) $6.7\ \Omega$
- (D) $27\ \Omega$

9. What is the voltage drop across R_1 in the circuit below?

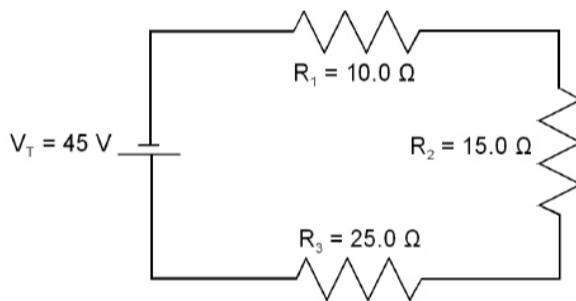- (A) $4.5\ \text{V}$
- (B) $9.0\ \text{V}$
- (C) $11\ \text{V}$
- (D) $15\ \text{V}$




10. What is the voltage drop across one of three identical resistors that are connected in series to a $6.0\ \text{V}$ source?

- (A) $2.0\ \text{V}$
- (B) $3.0\ \text{V}$
- (C) $6.0\ \text{V}$
- (D) $18\ \text{V}$

11. What is the voltage, V , across the source for the circuit below?

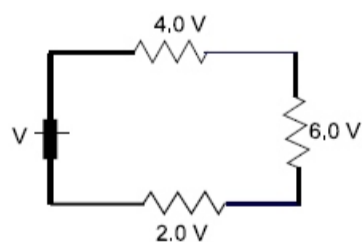- (A) $1.1\ \text{V}$
- (B) $4.0\ \text{V}$
- (C) $6.0\ \text{V}$
- (D) $12.0\ \text{V}$




12. Who proposed that around any closed path, the sum of the voltage rises is equal to the sum of the voltage drops?

- (A) Coulomb
- (B) Kirchoff
- (C) Ohm
- (D) Voltaire

13. What value of resistor, R , must be added in the circuit below to give a total resistance of $32\ \Omega$?

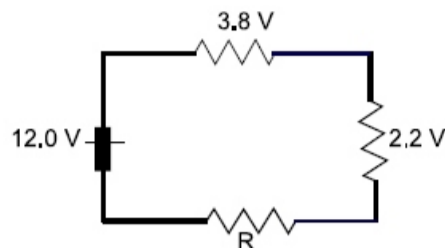- (A) $2.0\ \Omega$
 (B) $8.0\ \Omega$
 (C) $16\ \Omega$
 (D) $26\ \Omega$



14. If a $2.0\ \Omega$, $4.0\ \Omega$, and $6.0\ \Omega$ resistor are connected in series with a $24\ \text{V}$ battery, what is the potential difference across the $2.0\ \Omega$ resistor?

- (A) $4.0\ \text{V}$
 (B) $8.0\ \text{V}$
 (C) $12\ \text{V}$
 (D) $24\ \text{V}$


15. If a series circuit contains two $15\ \Omega$ light bulbs, three $25\ \Omega$ light bulbs, and a $24\ \text{V}$ battery, how much current passes through each bulb?

- (A) $0.15\ \text{A}$
 (B) $0.23\ \text{A}$
 (C) $0.60\ \text{A}$
 (D) $1.7\ \text{A}$


16. A string of 20 identical lights is connected in series across a $120\ \text{V}$ source, and each light consumes $2.4\ \text{W}$. What is the resistance of each bulb?

- (A) $6.0\ \Omega$
 (B) $15\ \Omega$
 (C) $48\ \Omega$
 (D) $120\ \Omega$

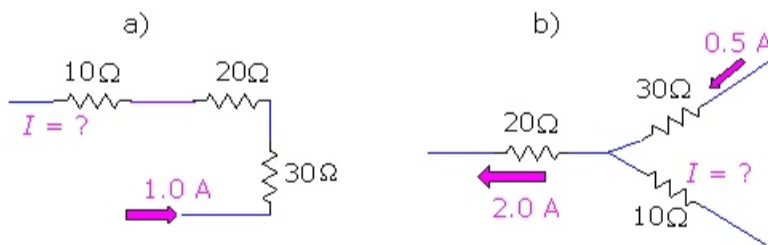
1. For the circuit branches shown, what is the current through the $10\ \Omega$ resistor? [2]



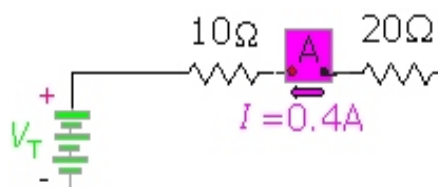2. An ammeter connected between the two resistors in the diagram to the right reads $0.4\ \text{A}$. What is the voltage of the battery? [2]



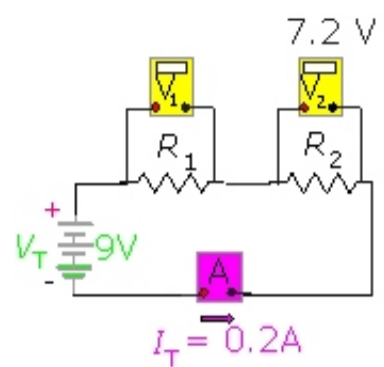3. According to the parameters in the circuit to the right, what is the value of R_1 ? [2]



4. Calculate each of the following:

(A) The equivalent resistance of three $8\ \Omega$ resistors in series [1]

(B) The total resistance of a series circuit is $76\ \Omega$. If two of the resistors are $22\ \Omega$ and $16\ \Omega$, what is the value of the third resistor? [2]