


Intermediate Science 9

Unit 3: CURRENT ELECTRICITY

WORKSHEET 1: ELECTRIC CURRENT AND CIRCUITS




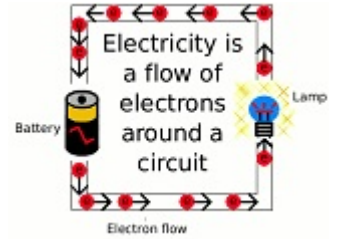Current Electricity: Electricity produced due to the flow of electric charge from one place to another in a conductor



Current (I) refers to the flow of charges in a circuit. It is the amount of charge passing a point every second. It is measured in Amperes or Amps (A).

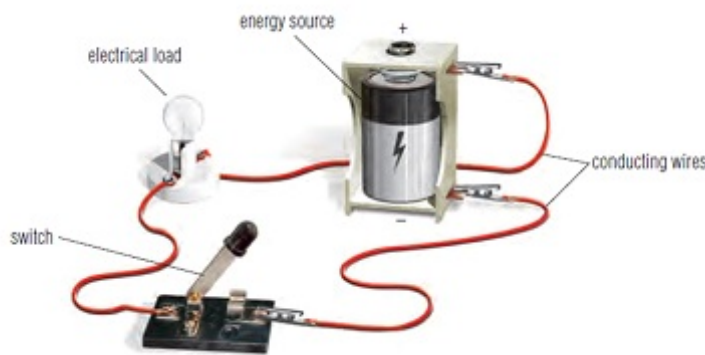
Electric Circuit: a complete pathway that allows electrons to flow from the source and back again



An electric circuit can be considered a system consisting of four subsystems:

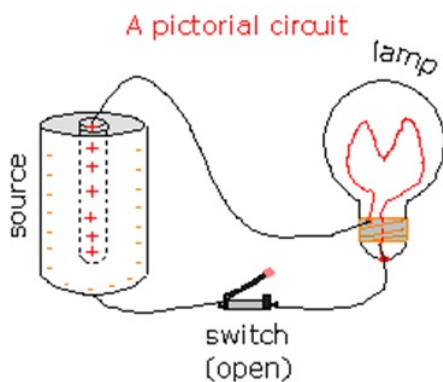1. **Source** a device which changes one type of energy into electrical energy, example a chemical cell or generator.
2. **Conductor** a material which allows electric current (electrons) to pass through it easily, example copper wire
3. **Control** starts and stops the flow of electrons in an electric circuit, example switch
4. **Load** the device which changes electrical energy into some other form of energy, example motor, light bulb

Schematic Diagram: a circuit diagram which shows the logic of the connections rather than the actual layout of the components. A diagram using graphic symbols to show how a circuit functions electrically.



Symbol	Component	Function
—	wire	conductor; allows electrons to flow
	cell, battery	electrical source; longer side is the positive terminal, shorter side is the negative terminal
	lamp (light bulb)	specific load; converts electricity to light and heat
	resistor	general load; converts electricity to heat
	switch	opens and closes the circuit
	ammeter	measures current through a device, connected in series
	voltmeter	measures voltage across a device, connected in parallel


RULES for Drawing Circuit Diagrams

- Always use a ruler to draw straight lines for the conducting wires
- Make right-angle corners (└) so that your finished diagrams is a rectangle
- Contain 4 basic parts: (1)Electrical source, (2) Switch, (3) Load, (4) -Conducting wire

Open Circuit And Closed Circuit


Open circuit: when the flow of electrons is interrupted and the electrons cannot move through the circuit. (Switch is Opened)

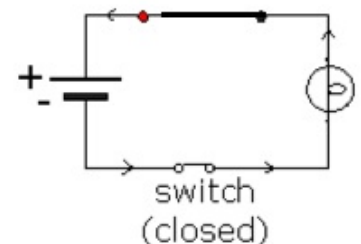Closed Circuit: when there is a flow of electrons throughout the circuit. (Switch Closed)




Series Circuit and Parallel Circuit:

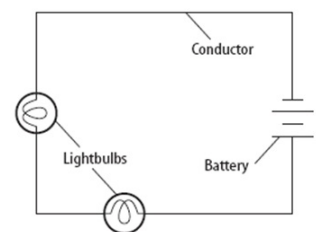Series circuit: provides a single pathway for the current to flow. If the circuit breaks, all devices using the circuit will fail.



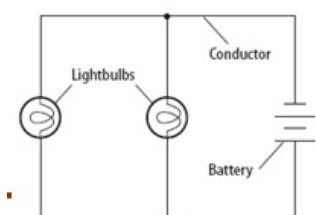Parallel Circuit: has multiple pathways for the current to flow. If the circuit is broken the current may pass through other pathways and other devices will continue to work.



PART A: MULTIPLE CHOICE

- Which of the following describes the flow of electrons around a circuit?
 - Conductor
 - Current Electricity
 - Insulator
 - Static Electricity
- Which term below refers to the flow of charges in a circuit?
 - Circuit
 - Current
 - Load
 - Source
- What unit is used to measure current?
 - Amperes (A)
 - Coulomb (C)
 - Meter (m)
 - Voltage (V)
- How would you describe current?
 - The amount of electrons passing a point in a given time
 - The amount of protons passing a point in a given time
 - The number of electrons at rest in a circuit
 - The number of protons at rest in a circuit
- What is an electric circuit?
 - An incomplete pathway that allows electrons to flow from the source and back again
 - A complete pathway that allows electrons to flow from the source and back again
 - A complete pathway that allows protons to flow from the source and back again
 - An incomplete pathway that allows protons to flow from the source and back again
- Which of the following is required to build a complete electric circuit?
 - Source
 - Conductor
 - Control (switch)
 - Load
 - (I) only
 - (I) and (II)
 - (I), (II), and (III)
 - (I), (II), and (III) and (IV)
- Which of the following refers to an electric device that changes electrical energy into some other form?
 - Source
 - Conductor
 - Control (switch)
 - Load


8. What is shown in the picture to the right?

- (A) Source
- (B) Conductor
- (C) Control (switch)
- (D) Load




9. What is shown in the picture to the right?

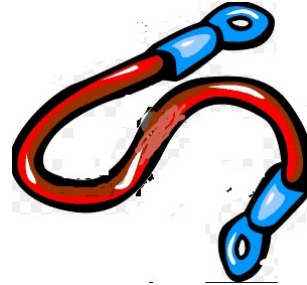- (A) Source
- (B) Conductor
- (C) Control (switch)
- (D) Load



10. What is depicted in the picture to the right?

- (A) Cell
- (B) Lamp
- (C) Ammeter
- (D) Wire

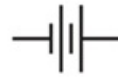
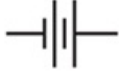




11. What is depicted in the picture to the right?

- (A) Cell
- (B) Lamp
- (C) Ammeter
- (D) Wire




12. Which of the following is a symbol for a resistor?

(A)	
(B)	
(C)	
(D)	

13. Which of the following best describes an open circuit?
- (A) The flow of electrons is uninterrupted and the electrons can move through the circuit
 - (B) The flow of electrons is interrupted and the electrons can move through the circuit
 - (C) The flow of electrons is uninterrupted and the electrons cannot move through the circuit
 - (D) The flow of electrons is interrupted and the electrons cannot move through the circuit

14. What is illustrated in the below picture?

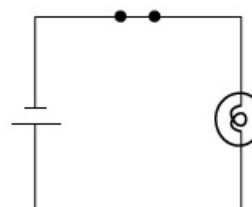- (A) Closed circuit
- (B) Fried circuit
- (C) Open circuit
- (D) Parallel circuit




15. Which of the following is the best definition of a series circuit?

- (A) Provides a single pathway for the current to flow.
- (B) Provides multiple pathways for the current to flow
- (C) All devices using the circuit will continue to work if the current is interrupted anywhere in the circuit
- (D) Only some devices using the circuit will continue to work if the current is interrupted anywhere in the circuit

16. What type of circuit is shown below?

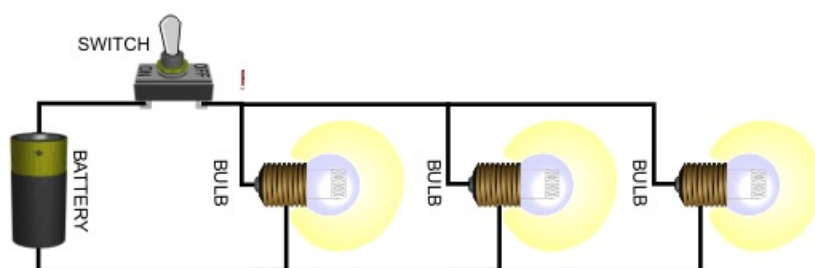- (A) Fired circuit
- (B) Series circuit
- (C) Open circuit
- (D) Parallel circuit



17. What device is used to measure current?

- (A) Ammeter
- (B) Odometer
- (C) Thermometer
- (D) Voltmeter

18. How should an ammeter be placed in an electric circuit?

- (A) Parallel
- (B) Series
- (C) Parallel or series
- (D) Diagonal

1. Define electric current. What units are used to measure current?

2. (A) Define electric circuit.

3. Distinguish between an open and closed circuit.

4. Distinguish between a series and parallel circuit.

5. Explain the difference between static electricity and current electricity.

Static Electricity	Current Electricity
