

Intermediate Science 9

Unit 3: CURRENT ELECTRICITY

WORKSHEET 4: OHM'S LAW




Georg Simon Ohm (1789-1854): Discovered the mathematical relationship between current, voltage, and resistance.




Ohm's Law

$$V = IR$$

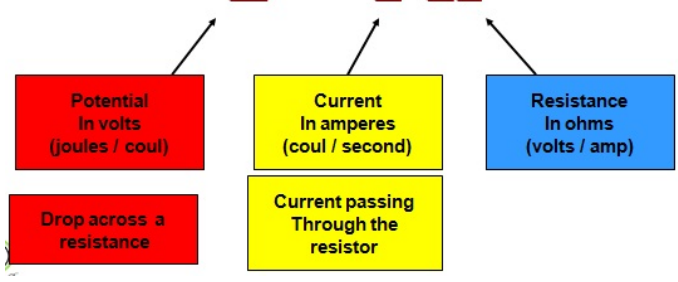

A triangle can be used to rearrange this equation:

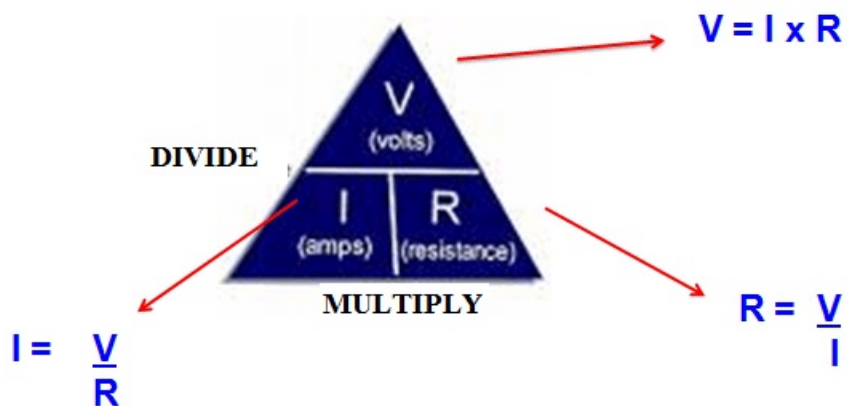

Example 1: Find Voltage

If a circuit has 2A of current running through it and the total resistance in the circuit is 19Ω , then what is the total voltage?

Example 2: Find Voltage

A circuit uses 0.5A of current and has total resistance of 18Ω . How much voltage is the circuit supplied with?

Example 3: Find Current

A toaster oven has a resistance of 12 ohms and is plugged into a 120-volt outlet. How much current does it draw?

Example 4 : Find Current

A house is supplied with voltage of 120V. If the total resistance is 60Ω how much current is running through the wires?

Example 5: Find Resistance

A circuit is supplied with 15V of voltage and has current of 3A. What is the total resistance in the circuit?

Example 6: Find Resistance

If a computer uses 5A of current and is supplied with 120V of voltage, then what is the total resistance of the computer?

Example 7: Complete the following chart:

Ohms	Volts	Amps
	100	25
	150	10
	30	15
9		5
6	48	

PART A: MULTIPLE CHOICE

1. In Ohm's Law, what does the symbol I represent?
 - (A) Current
 - (B) Load
 - (C) Power
 - (D) Voltage

2. Which of the following would not be an equation from Ohm's Law
 - (A) $V = \frac{I}{R}$
 - (B) $V = IR$
 - (C) $R = \frac{V}{I}$
 - (D) $I = \frac{V}{R}$


3. The current through a heater is 12 A when it is plugged into a 120 V source. What is the resistance of the heater?
 - (A) 0.10 Ω
 - (B) 10 Ω
 - (C) 132 Ω
 - (D) 1440 Ω

4. If 0.05 A of current flows through a 40 Ω light bulb, what voltage is dropped across the light bulb?
 - (A) 0.00125 V
 - (B) 2.0 V
 - (C) 40.05 V
 - (D) 800 V

5. What potential difference must be applied to a 26 Ω resistor to cause a current of 0.50 A to flow through it?
 - (A) 6.5 V
 - (B) 13 V
 - (C) 26 V
 - (D) 52 V

6. Using Ohm's law, what is the current drawn from a 12V battery if the circuit contains 5.5 ohms of resistance?
 - (A) 6.5A
 - (B) 0.46A
 - (C) 66A
 - (D) 2.18A

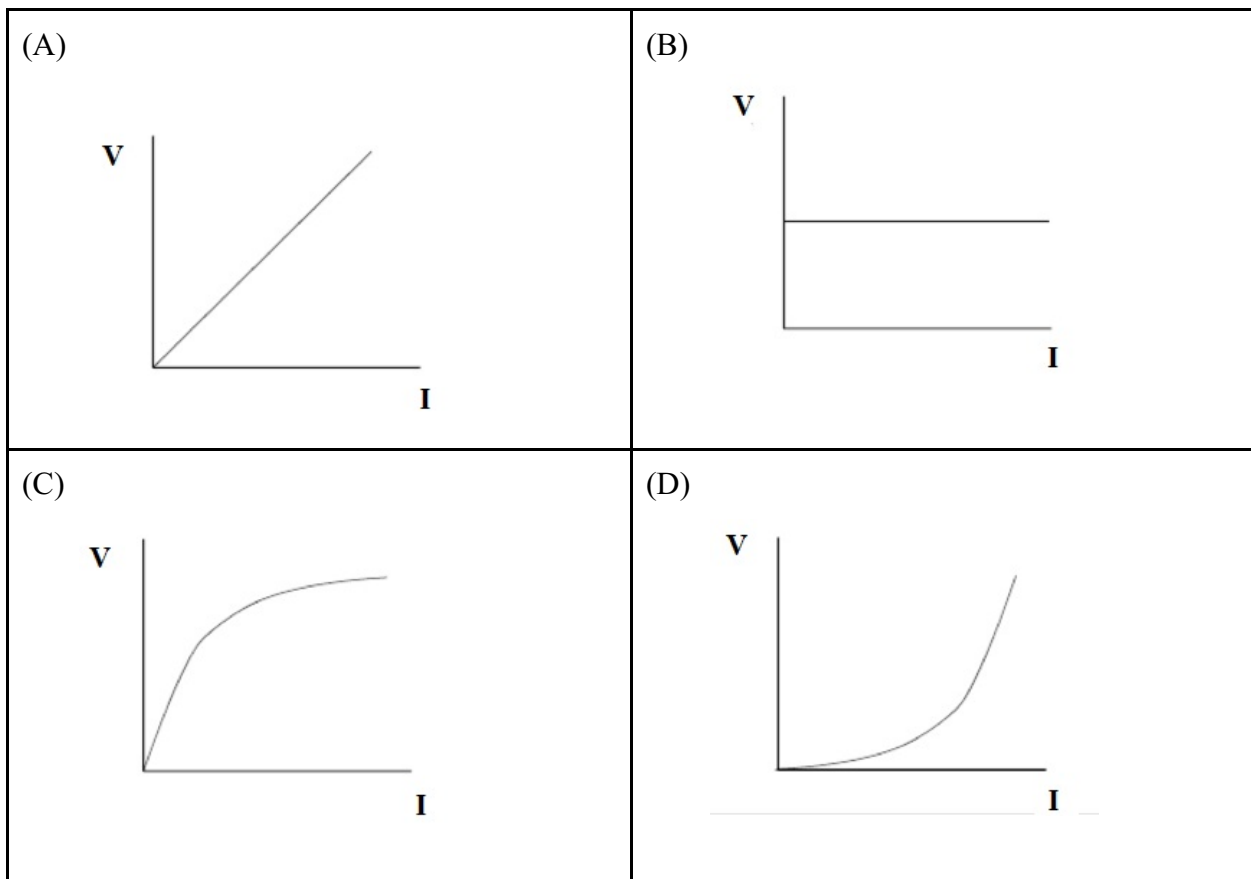7. A 2.3A current is drawn from a 24V battery. What is the resistance of the circuit?
- (A) 10.4 Ω
 (B) 55.2 Ω
 (C) 0.095 Ω
 (D) 21.7 Ω
8. Using Ohm's law, what is the voltage of a circuit with 2.4 ohms of resistance and a current of 4A?
- (A) 1.67 V
 (B) 0.6 V
 (C) 9.6 V
 (D) 1.2 V
9. Using ohms law, calculate the current in a circuit with 3, 1.5 V batteries and 10 Ω of resistance:
- (A) 0.15 A
 (B) 6.67 A
 (C) 0.45A
 (D) 15A
10. Which graph illustrates Ohm's Law?



PART B: WRITTEN RESPONSE

1. How much current is in a circuit that includes a 9 volt battery and a bulb with a resistance of 3 ohms?
2. A circuit contains two 1.5 volt batteries and a bulb with a resistance of 3 ohms. Calculate the current.
3. What is the voltage of a circuit with 15 A of current and toaster with 8 Ω of resistance?
4. A light bulb has a resistance of 4 Ω and a current of 2 A. What is the voltage across the bulb?
5. How many ohms of resistance must be present in a circuit that has 120 V and a current of 10 A?
6. An alarm clock draws 0.5 A of current when connected to a 120 V circuit. Calculate its resistance.
7. A portable CD player uses two 1.5 V batteries. If the current in the CD player is 2 A, what is its resistance?
8. You have a large flashlight that takes 4 D-cell batteries. If the current in the flashlight is 2 amps, what is the resistance of the light bulb? (Hint: A D-cell battery has 1.5 volts.)